



1. OR Gate

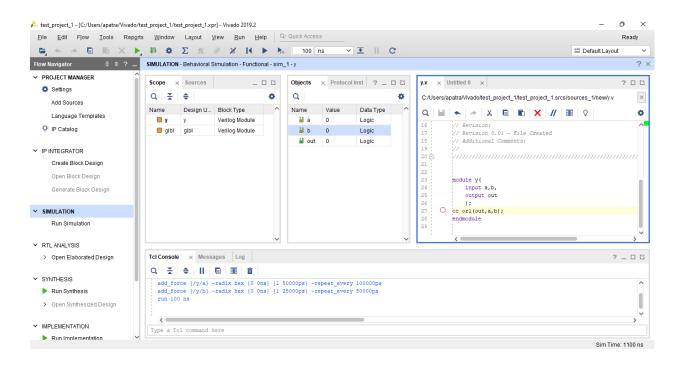

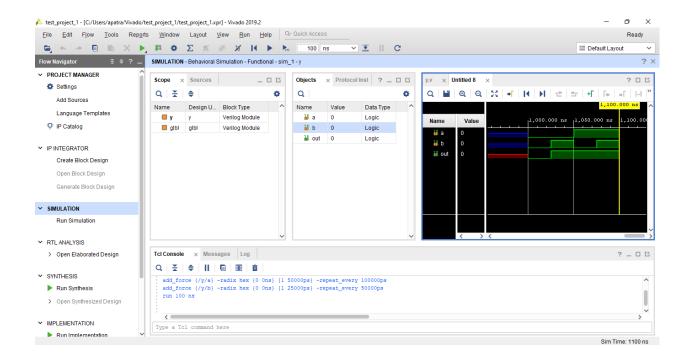



2. AND Gate

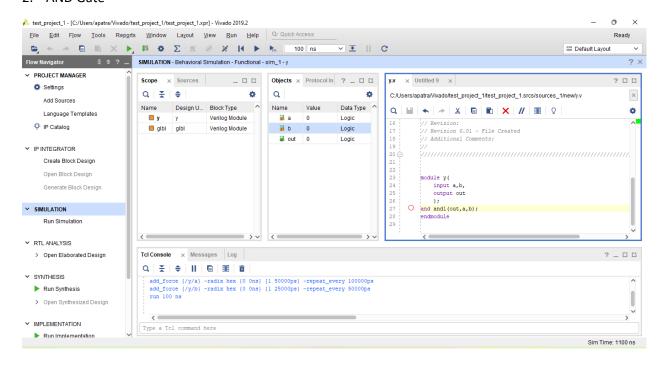

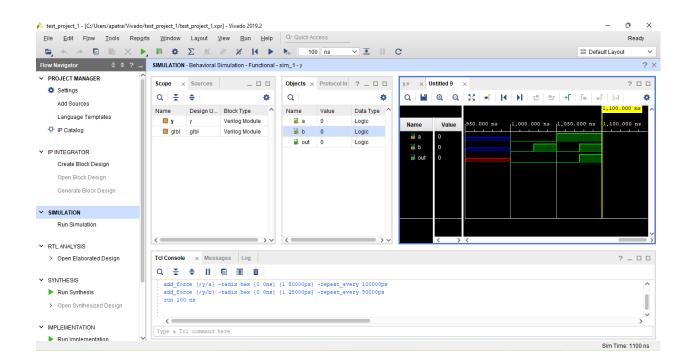


3. NOR Gate

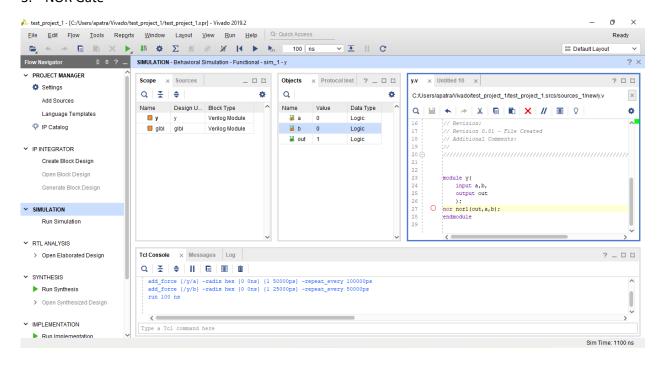


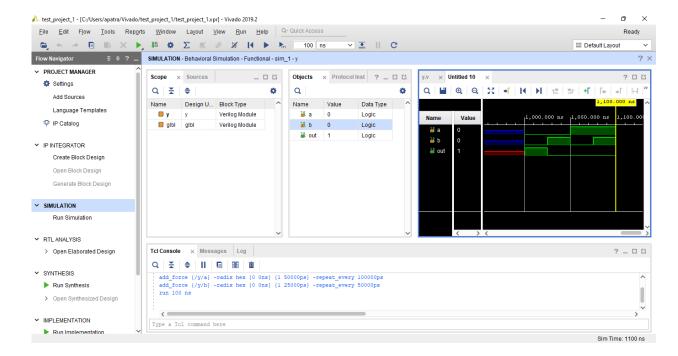


4. NAND Gate

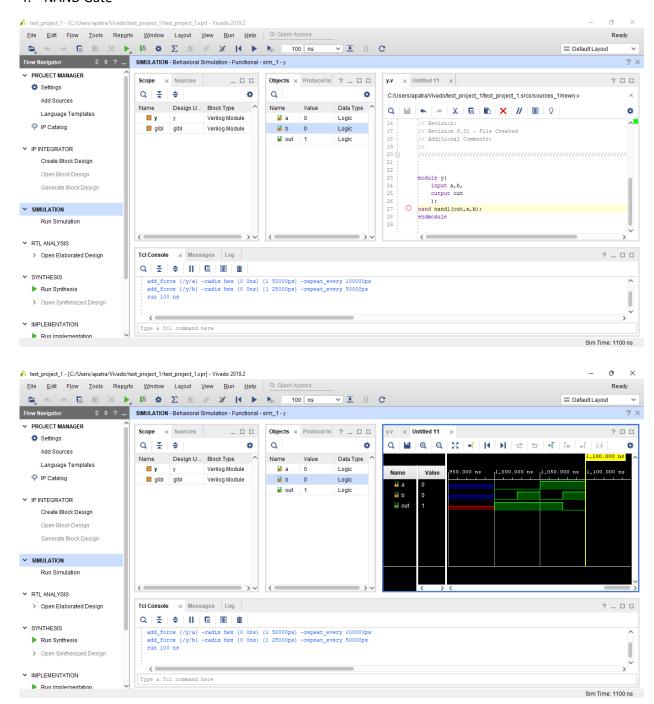

5. XOR Gate

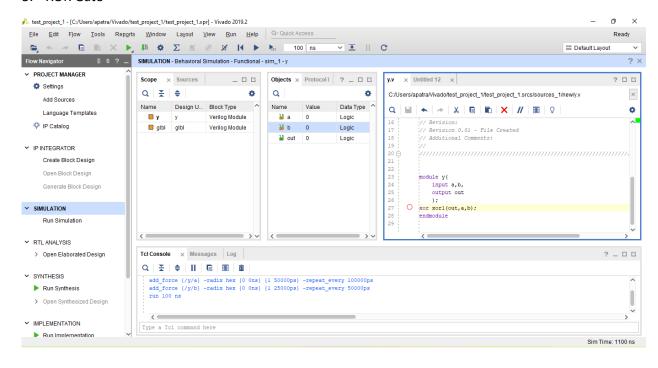

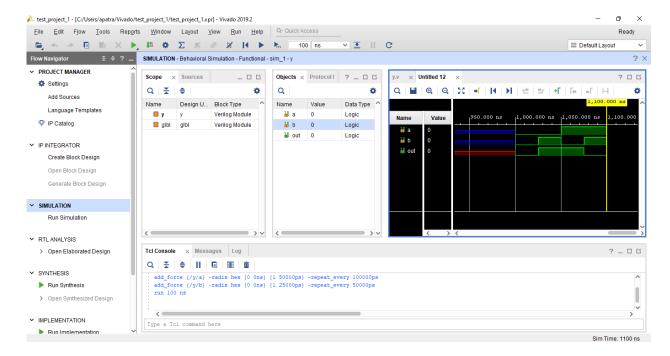

6. NOT Gate

